



# Arithmetic and Logic Unit Second Part

## Arquitectura de Computadoras

Arturo Díaz Pérez

Centro de Investigación y de Estudios Avanzados del IPN

Laboratorio de Tecnologías de Información

[adiaz@cinvestav.mx](mailto:adiaz@cinvestav.mx)



# Multiplication

- ♦ Multiplication can't be that hard!
  - It's just repeated addition.
  - If we have adders, we can do multiplication also.
- ♦ Remember that the AND operation is equivalent to multiplication on two bits:

a	b	ab
0	0	0
0	1	0
1	0	0
1	1	1

a	b	$a \times b$
0	0	0
0	1	0
1	0	0
1	1	1



# Binary multiplication example

				1	1	0	1	Multiplicand
			x	0	1	1	0	Multiplier
				0	0	0	0	Partial products
			1	1	0	1		
		1	1	0	1			
	1	0	0	0	0			
+	0	0	0	0				
	1	0	0	1	1	1	0	Product


- ◆ Since we always multiply by either 0 or 1, the **partial products** are always either **0000** or the multiplicand (**1101** in this example).
- ◆ There are four partial products which are added to form the result.
  - We can add them in pairs, using three adders.
  - Even though the product has up to 8 bits, we can use 4-bit adders if we “stagger” them leftwards, like the partial products themselves.


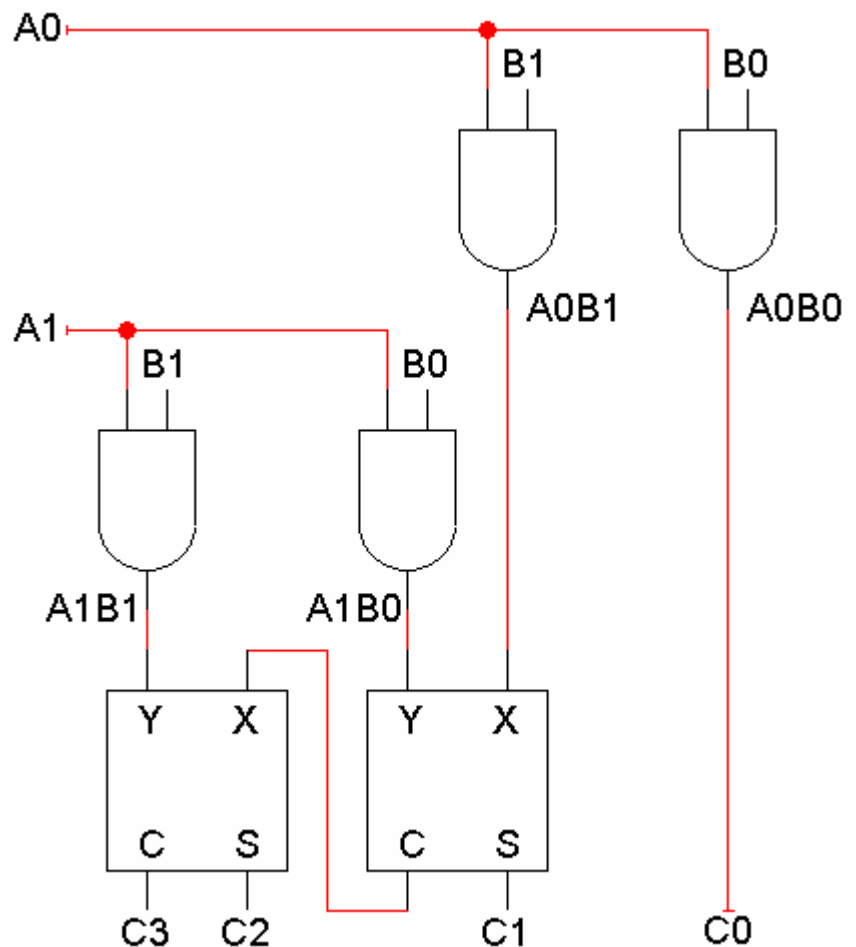
# A 2x2 binary multiplier

- ♦ The AND gates produce the partial products.
- ♦ For a 2-bit by 2-bit multiplier, we can just use two half adders to sum the partial products. In general, though, we'll need full adders.
- ♦ Here  $C_3$ - $C_0$  are the product, not carries!


$$\begin{array}{r} \phantom{+} \phantom{A_1B_1} \phantom{A_1B_0} \phantom{A_0B_1} \phantom{A_0B_0} \\ \phantom{+} \phantom{A_1B_1} \phantom{A_1B_0} \phantom{A_0B_1} \phantom{A_0B_0} \\ \phantom{+} \phantom{A_1B_1} \phantom{A_1B_0} \phantom{A_0B_1} \phantom{A_0B_0} \\ \phantom{+} \phantom{A_1B_1} \phantom{A_1B_0} \phantom{A_0B_1} \phantom{A_0B_0} \\ \hline + \phantom{A_1B_1} \phantom{A_1B_0} \phantom{A_0B_1} \phantom{A_0B_0} \\ \hline \phantom{C_3} \phantom{C_2} \phantom{C_1} \phantom{C_0} \\ \hline C_3 \phantom{C_2} \phantom{C_1} \phantom{C_0} \phantom{C_0} \end{array}$$


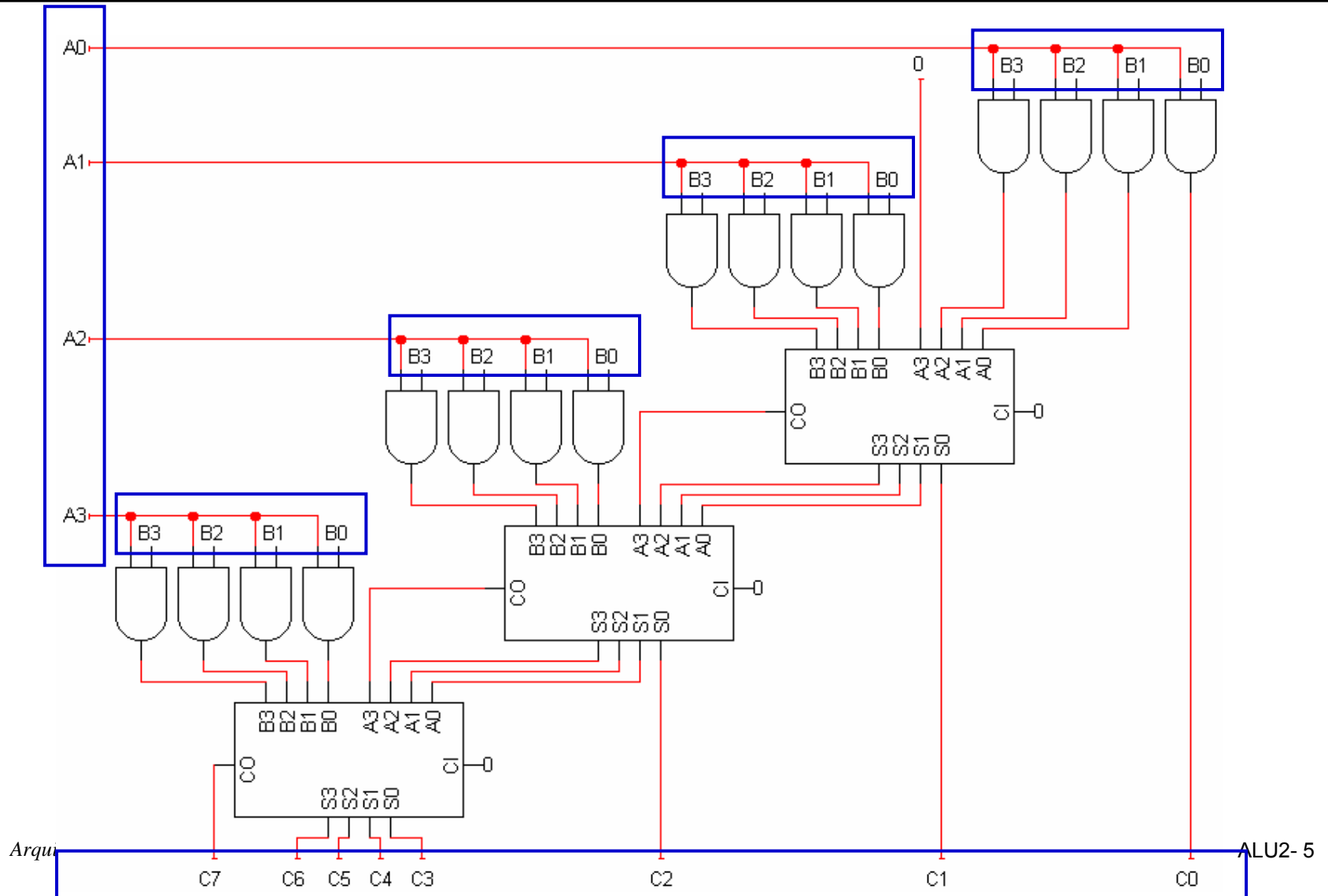
# A 4x4 multiplier circuit



Laboratorio de  
Tecnologías de Información





# More on multipliers

- ◆ Notice that this 4-bit multiplier produces an 8-bit result
  - We could just keep all 8 bits
  - Or, if we needed a 4-bit result, we could ignore C4-C7, and consider it an overflow condition if the result is longer than 4 bits
- ◆ Multipliers are very complex circuits.
  - In general, when multiplying an  $m$ -bit number by an  $n$ -bit number:
    - » There are  $n$  partial products, one for each bit of the multiplier
    - » This requires  $n-1$  adders, each of which can add  $m$  bits (the size of the multiplicand)
  - The circuit for 32-bit or 64-bit multiplication would be huge!

# Multiplication: a special case

- ◆ In decimal, an easy way to multiply by 10 is to shift all the digits to the left, and tack a 0 to the right end.

$$128 \times 10 = 1280$$

- ◆ We can do the same thing in binary. Shifting left is equivalent to multiplying by 2:

$$11 \times 10 = 110 \quad (\text{in decimal, } 3 \times 2 = 6)$$

- ◆ Shifting left twice is equivalent to multiplying by 4:

$$11 \times 100 = 1100 \quad (\text{in decimal, } 3 \times 4 = 12)$$

- ◆ As an aside, shifting to the *right* is equivalent to *dividing* by 2.

$$110 \div 10 = 11 \quad (\text{in decimal, } 6 \div 2 = 3)$$

# Addition and multiplication summary

---


- ◆ Adder and multiplier circuits mimic human algorithms for addition and multiplication
- ◆ Adders and multipliers are built hierarchically
  - We start with half adders or full adders and work our way up
  - Building these functions from scratch with truth tables and K-maps would be pretty difficult
- ◆ The arithmetic circuits impose a limit on the number of bits that can be added. Exceeding this limit results in overflow
- ◆ There is a tradeoff between simple but slow circuits (ripple carry adders) and complex but fast circuits (carry lookahead adders)
- ◆ Multiplication and division by powers of 2 can be handled with simple shifting


 
# Unsigned Combinational Multiplier




Laboratorio de  
Tecnologías de Información



- ◆ Stage  $i$  accumulates  $A * 2^i$  if  $B_i == 1$
- ◆ Q: How much hardware for 32 bit multiplier? Critical path?



# How does it work?

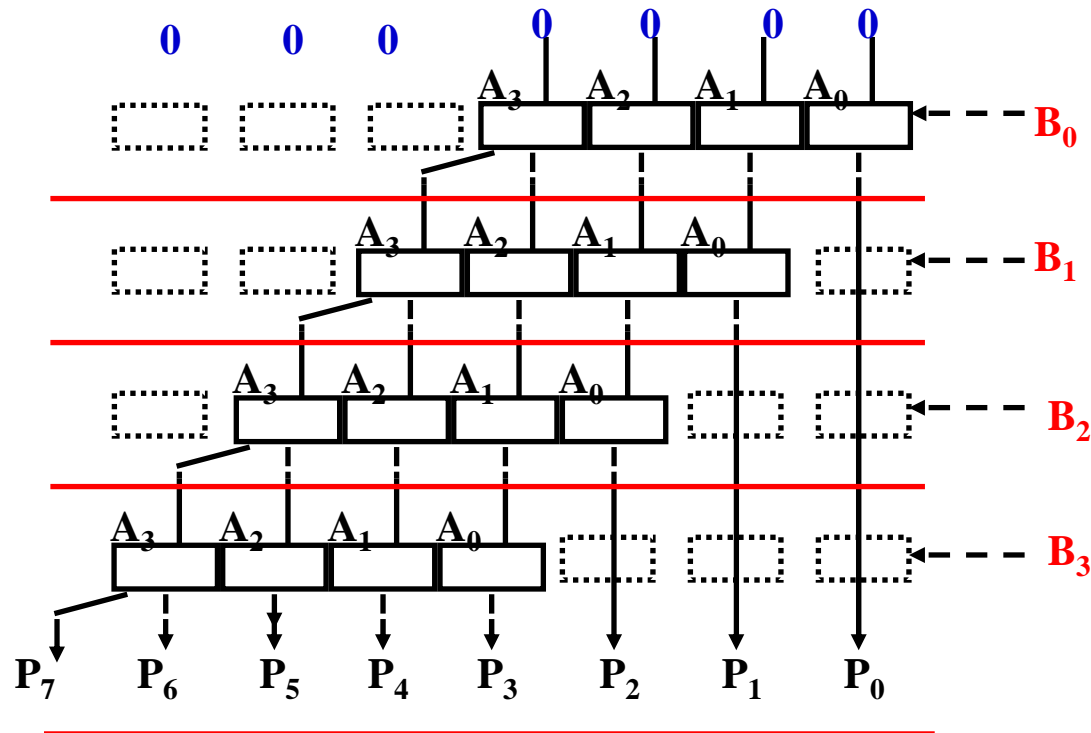


- ◆ at each stage shift A left (  $\times 2$  )
- ◆ use next bit of B to determine whether to add in shifted multiplicand
- ◆ accumulate 2n bit partial product at each stage
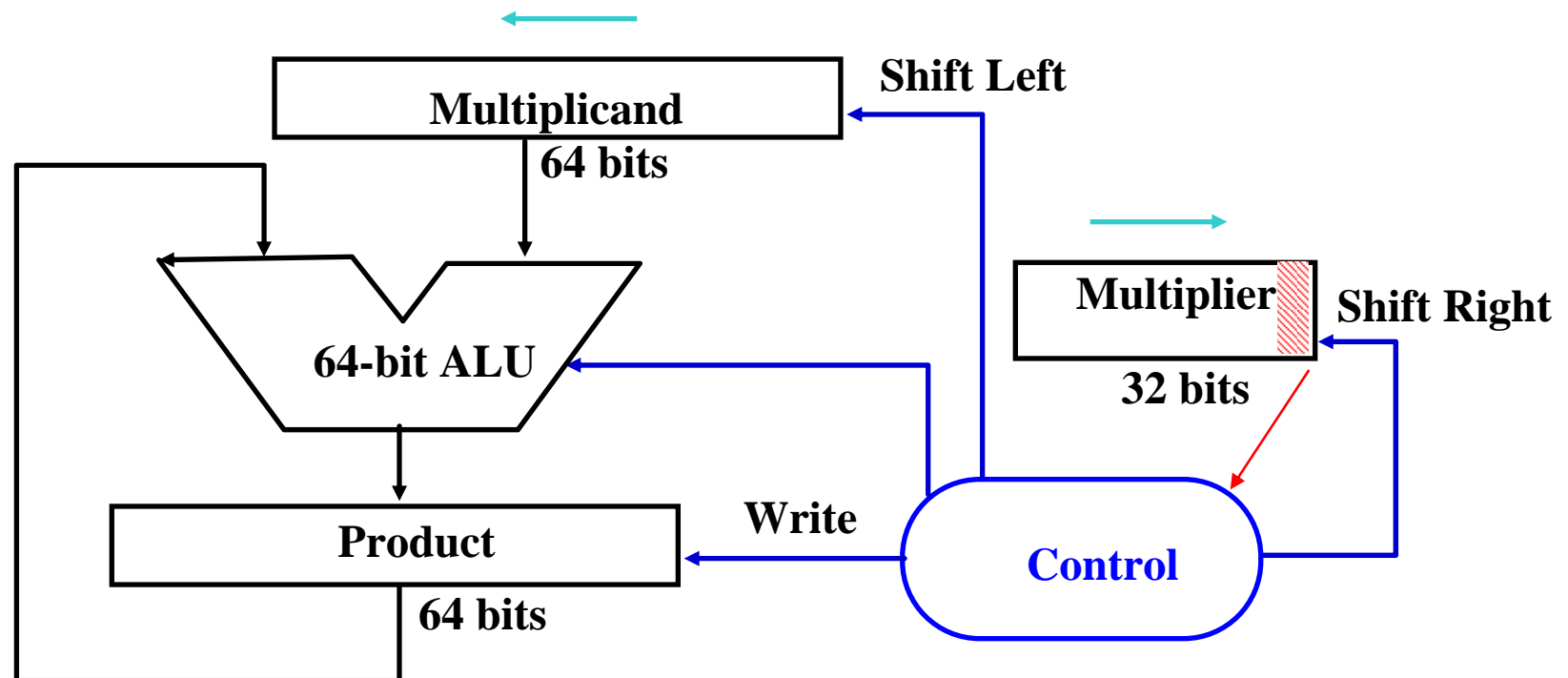
# Unsigned shift-add multiplier (version 1)



Laboratorio de  
Tecnologías de Información


- ◆ 64-bit Multiplicand reg, 64-bit ALU, 64-bit Product reg, 32-bit multiplier reg



**Multiplier = datapath + control**



# Multiply Algorithm Version 1

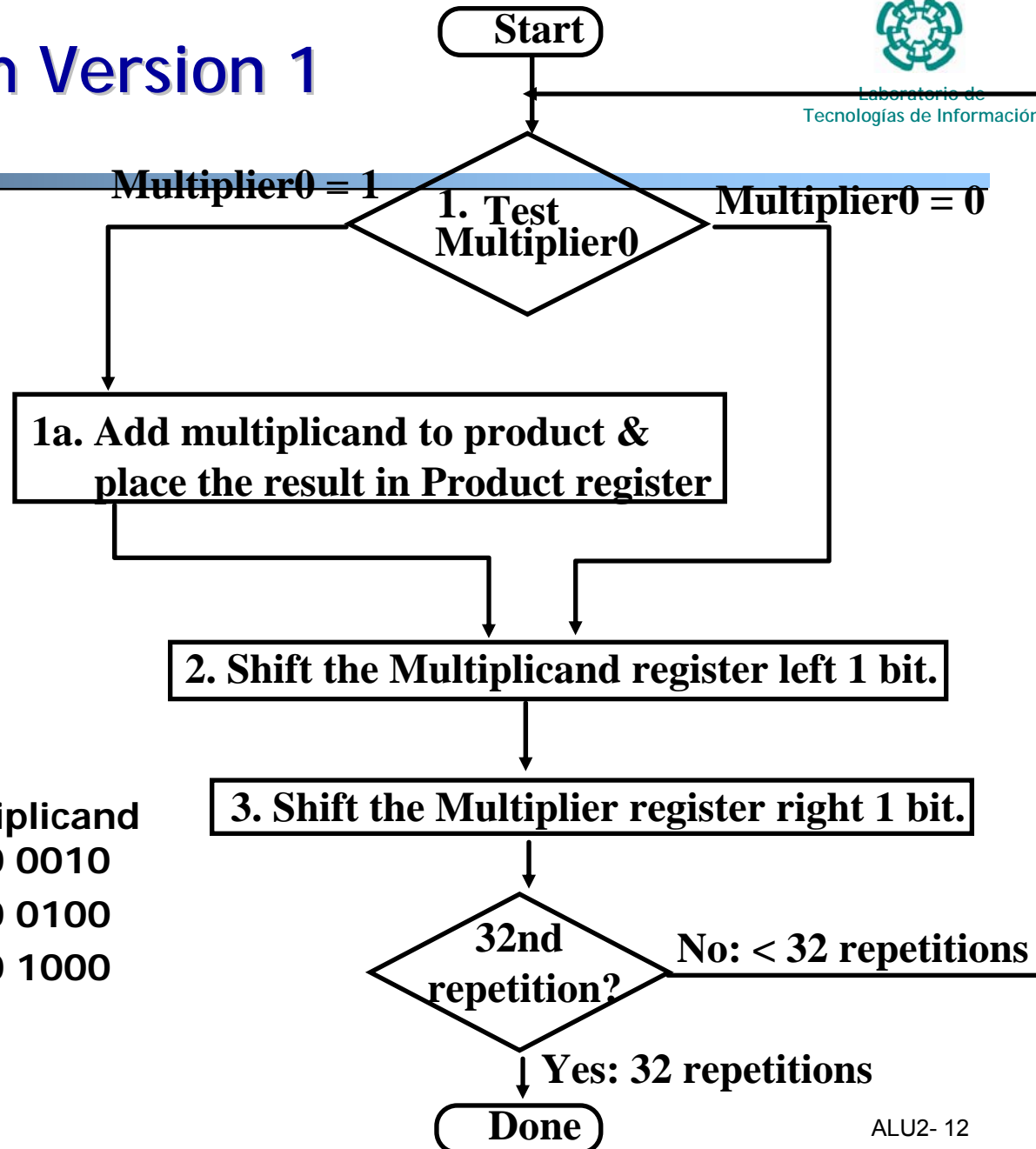

Product	Multiplier	Multiplicand
0000 0000	0011	0000 0010
0000 0010	0001	0000 0100
0000 0110	0000	0000 1000
0000 0110		

# Observations on Multiply Version 1



Laboratorio de  
Tecnologías de Información


- ◆ 1 clock per cycle  $\Rightarrow \approx 100$  clocks per multiply
  - Ratio of multiply to add 5:1 to 100:1
- ◆ Half of bits in multiplicand always 0  
 $\Rightarrow$  64-bit adder is wasted
- ◆ 0's inserted in left of multiplicand as shifted  
 $\Rightarrow$  least significant bits of product never changed once formed
- ◆ Instead of shifting multiplicand to left, shift product to right?
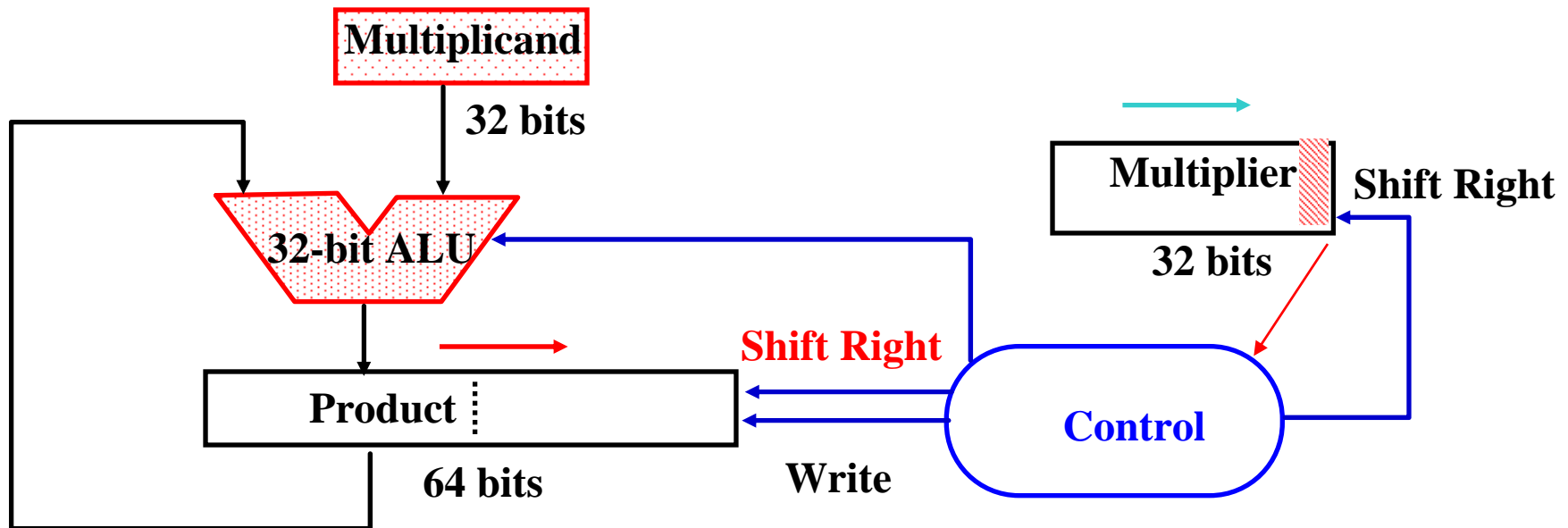
# MULTIPLY HARDWARE Version 2




Laboratorio de  
Tecnologías de Información


- ◆ 32-bit Multiplicand reg, 32-bit ALU, 64-bit Product reg, 32-bit Multiplier reg



 Remember original combinational multiplier:


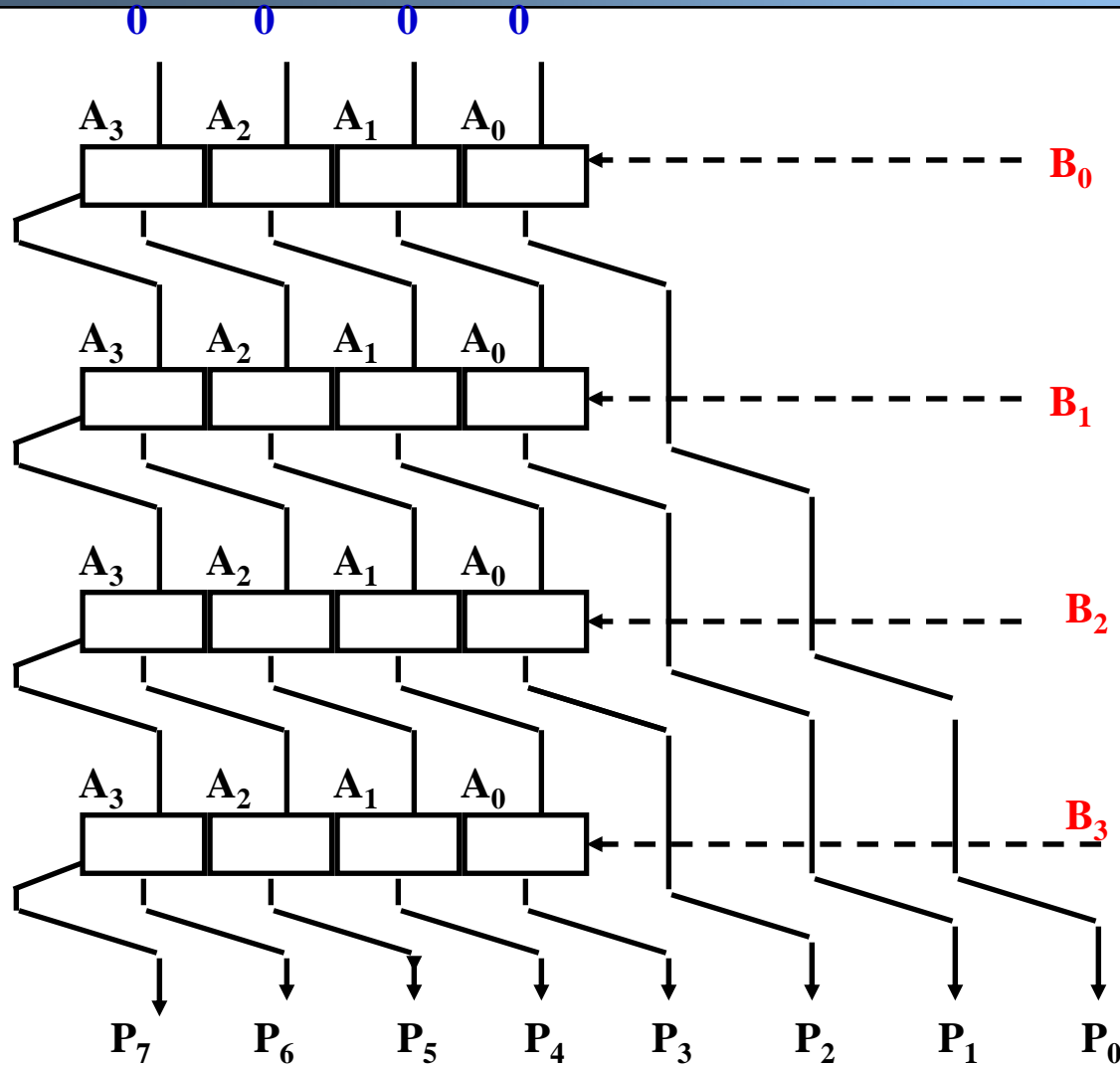
# Simply warp to let product move right...




- ◆ Multiplicand stay's still and product moves right


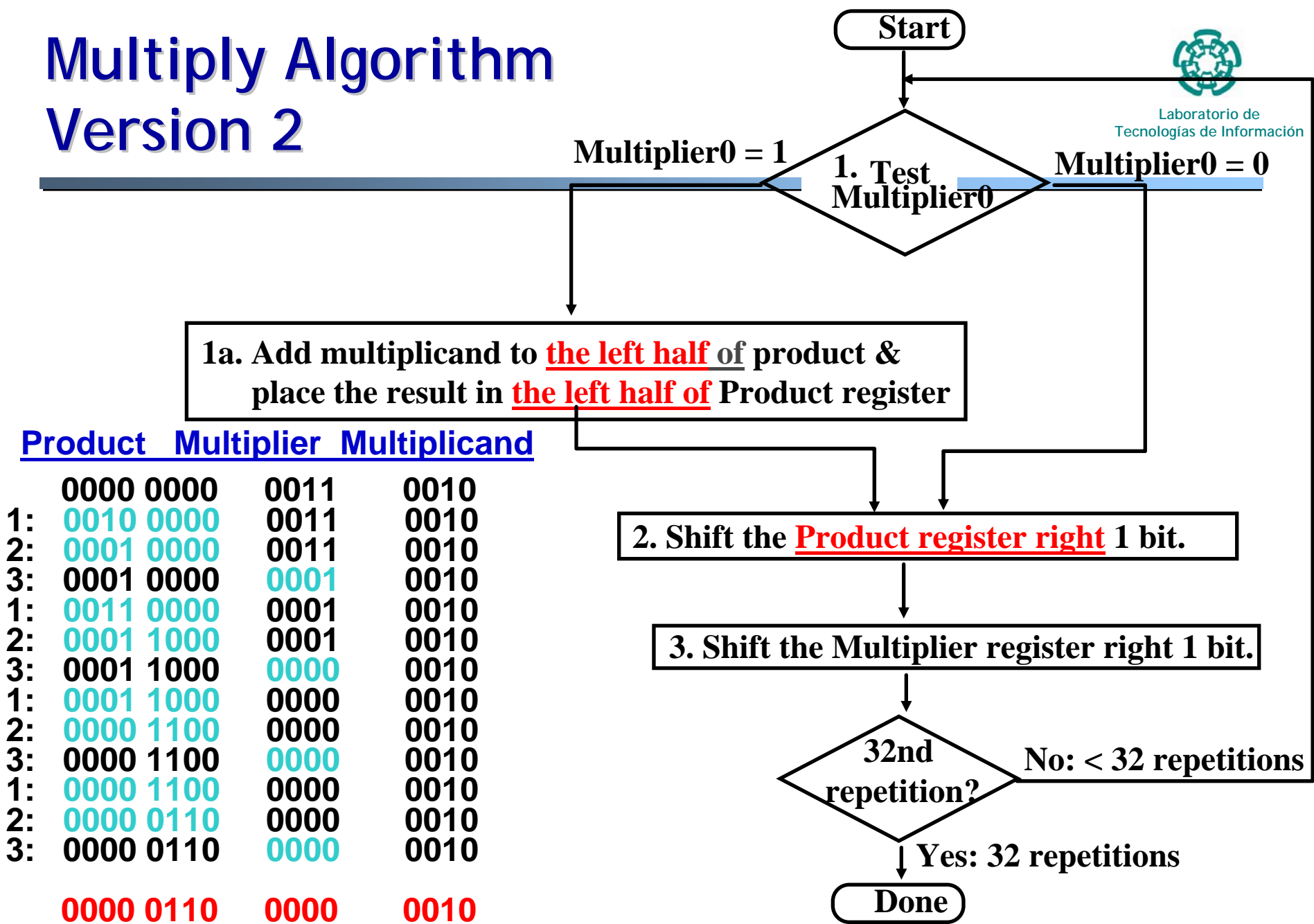
# Multiply Algorithm Version 2



Laboratorio de  
Tecnologías de Información





# Still more wasted space!

Multiplier0 = 1

1. Test  
Multiplier0

Multiplier0 = 0

1a. Add multiplicand to **the left half of** product &  
place the result in **the left half of** Product register

Product Multiplier Multiplicand

	0000	0000	0011	0010
1a:	0010	0000	0011	0010
2:	0001	0000	0011	0010
3:	0001	0000	0001	0010
1a:	0011	0000	0001	0010
2:	0001	1000	0001	0010
3:	0001	1000	0000	0010
1:	0001	1000	0000	0010
2:	0000	1100	0000	0010
3:	0000	1100	0000	0010
1:	0000	1100	0000	0010
2:	0000	0110	0000	0010
3:	0000	0110	0000	0010
	0000	0110	0000	0010

2. Shift the **Product register right** 1 bit.

3. Shift the Multiplier register right 1 bit.

32nd  
repetition?

No: < 32 repetitions

Yes: 32 repetitions

Done

# Observations on Multiply Version 2




Laboratorio de  
Tecnologías de Información

- ◆ Product register wastes space that exactly matches size of multiplier  
=> combine Multiplier register and Product register
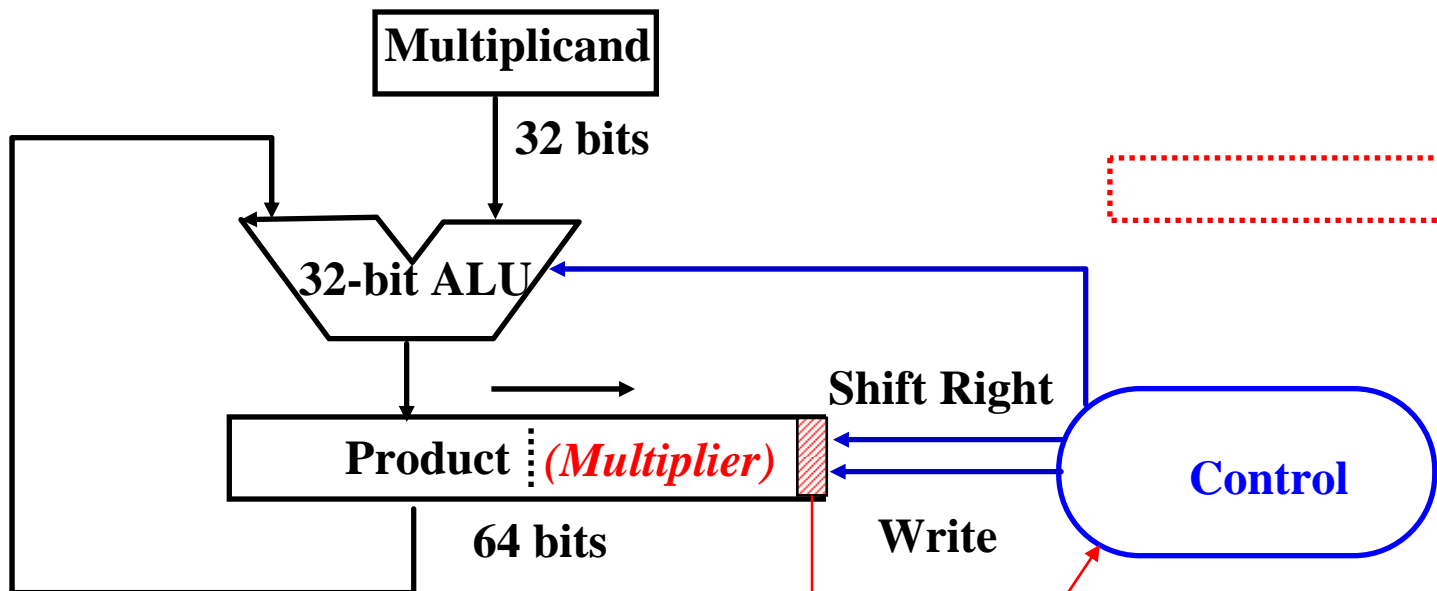
# MULTIPLY HARDWARE Version 3

- ◆ 32-bit Multiplicand reg, 32-bit ALU, 64-bit Product reg, (0-bit Multiplier reg)



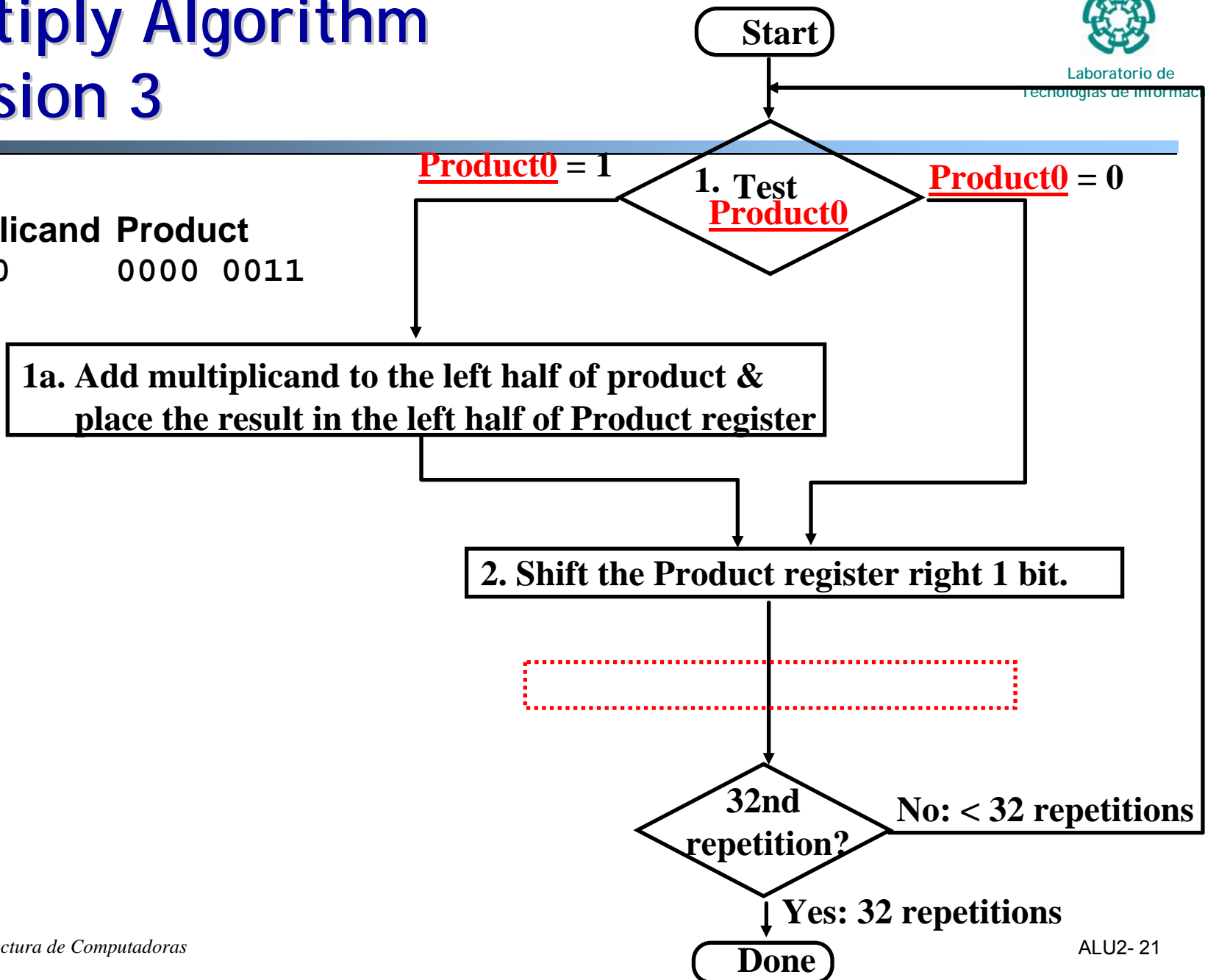
# Multiply Algorithm Version 3



Laboratorio de  
Tecnologías de Información

Multiplicand Product  
0010      0000 0011



# Observations on Multiply Version 3




Laboratorio de  
Tecnologías de Información

- ◆ 2 steps per bit because Multiplier & Product combined
- ◆ MIPS registers Hi and Lo are left and right half of Product
- ◆ Gives us MIPS instruction MultU
- ◆ How can you make it faster?
- ◆ What about signed multiplication?
  - easiest solution is to make both positive & remember whether to complement product when done (leave out the sign bit, run for 31 steps)
  - apply definition of 2's complement
    - » need to sign-extend partial products and subtract at the end
  - Booth's Algorithm is elegant way to multiply signed numbers using same hardware as before and save cycles
    - » can handle multiple bits at a time
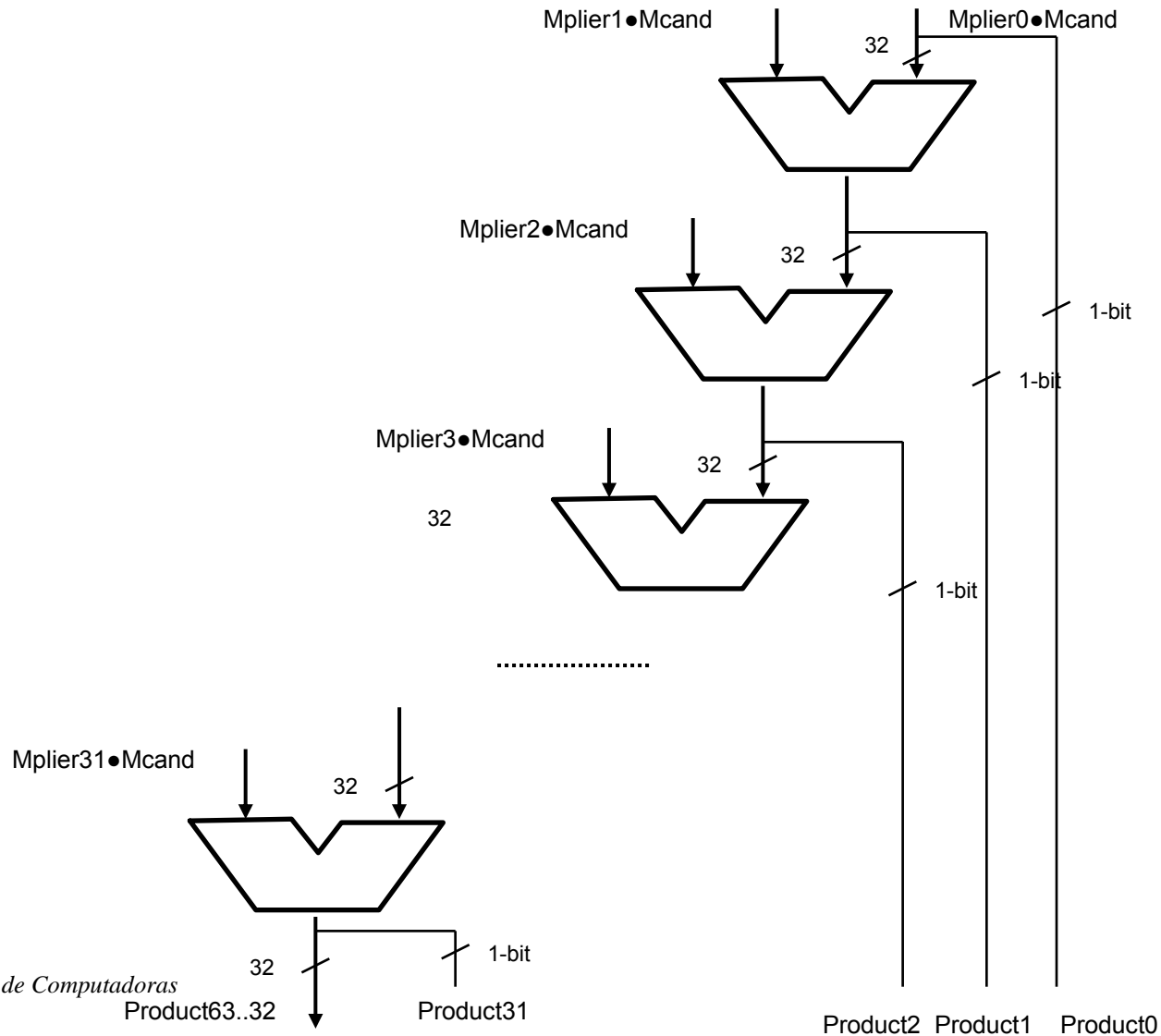
# Fast Multiplication Hardware



Laboratorio de  
Tecnologías de Información





# Divide: Paper & Pencil

	1001	Quotient
Divisor 1000	1001010	Dividend
	<u>-1000</u>	
	10	
	101	
	1010	
	<u>-1000</u>	
	10	Remainder (or Modulo result)

See how big a number can be subtracted, creating quotient bit on each step

Binary => 1 \* divisor or 0 \* divisor

Dividend = Quotient x Divisor + Remainder

=> | Dividend | = | Quotient | + | Divisor |


3 versions of divide, successive refinement





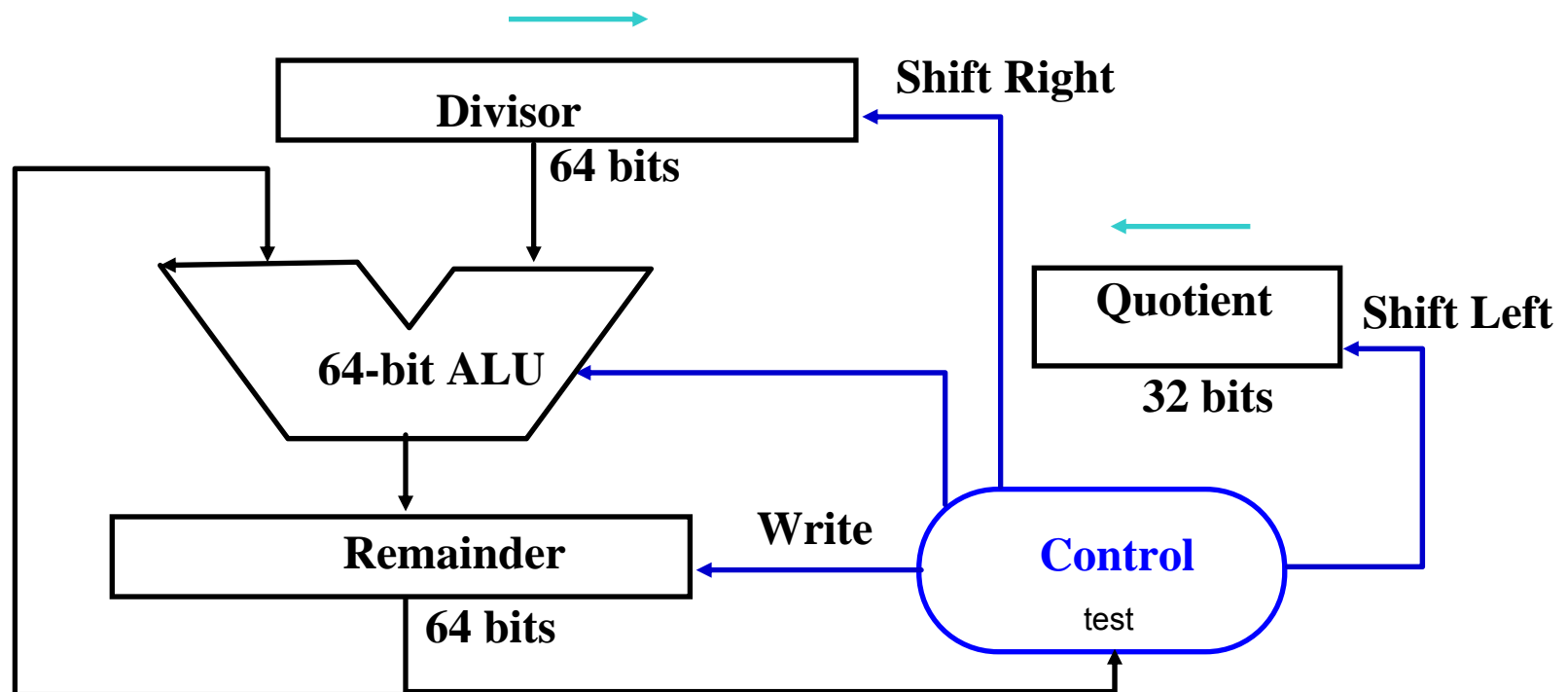
# DIVIDE HARDWARE Version 1

- ◆ 64-bit Divisor reg, 64-bit ALU, 64-bit Remainder reg, 32-bit Quotient reg



# Divide Algorithm Version 1

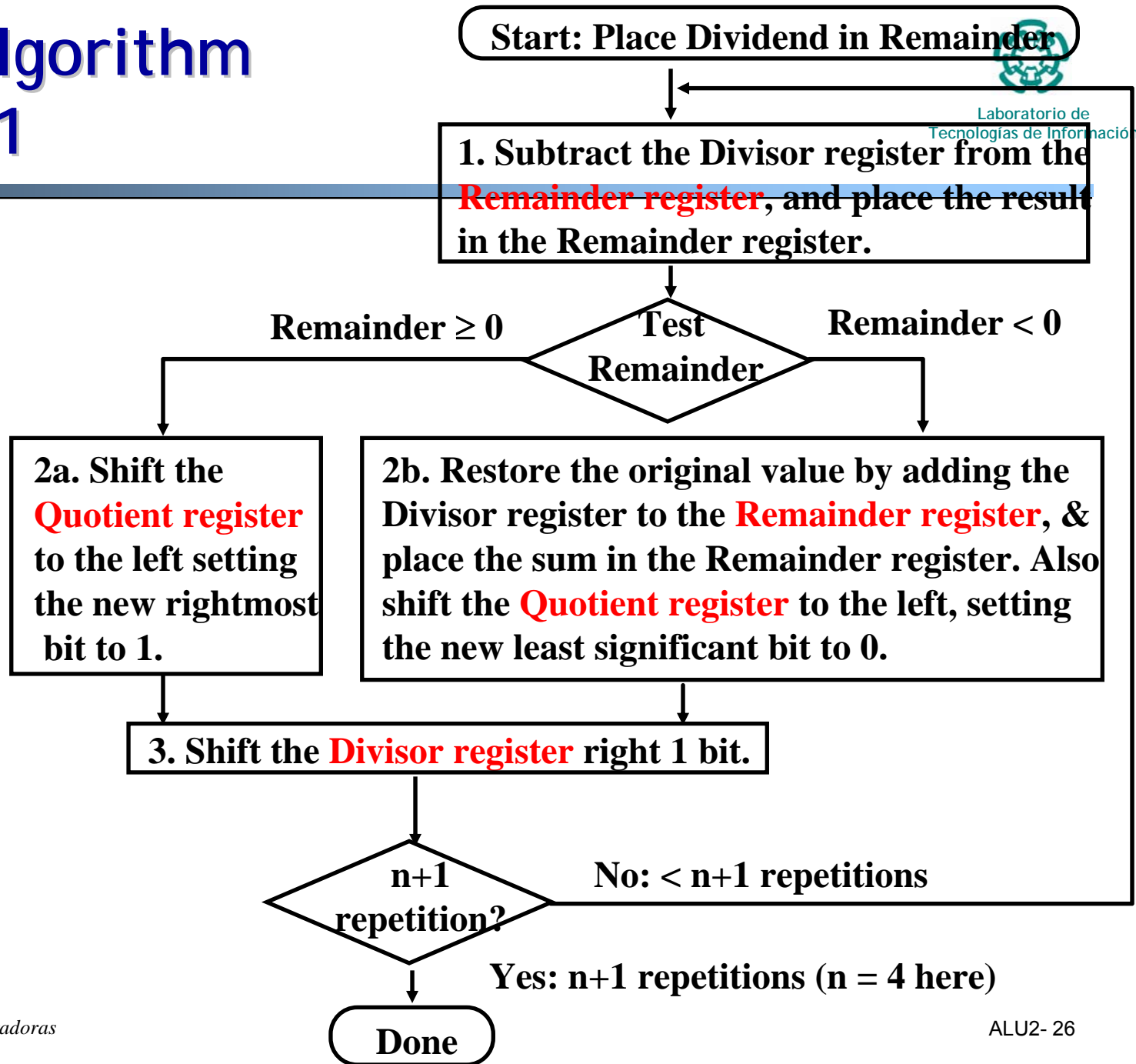

# Divide Algorithm Version 1



$$10 \overline{) 111}$$

	Quotient	Divisor		Remainder	
0: Initial Values	0000	0010	0000	0000	0111
1: Rem = Rem-Div	0000	0010	0000	①110	0111
2b: Rem<0; +Div, sll Q<-0	0000	0010	0000	0000	0111
3: Shift Div Right	0000	0001	0000	0000	0111
1: Rem = Rem-Div	0000	0001	0000	①111	0111
2b: Rem<0; +Div, sll Q<-0	0000	0001	0000	0000	0111
3: Shift Div Right	0000	0000	1000	0000	0111
1: Rem = Rem-Div	0000	0000	1000	①111	1111
2b: Rem<0; +Div, sll Q<-0	0000	0000	1000	0000	0111
3: Shift Div Right	0000	0000	0100	0000	0111
1: Rem = Rem-Div	0000	0000	0100	0000	0011
2a: Rem>=0; sll Q <-1	0001	0000	0100	①000	0011
3: Shift Div Right	0001	0000	0010	0000	0011
1: Rem = Rem-Div	0001	0000	0010	0000	0001
2a: Rem>=0; sll Q <-1	0011	0000	0010	①000	0001
3: Shift Div Right	0011	0000	0001	0000	0001

# Observations on Divide Version 1


---

- ◆ Half of bits in divisor always 0  
=> half of 64-bit adder is wasted  
=> half of divisor is wasted
- ◆ Instead of shifting divisor to right,  
shift remainder to left?
- ◆ 1st step cannot produce a 1 in quotient bit  
(otherwise too big)  
=> switch order to shift first and then subtract,  
can save 1 iteration



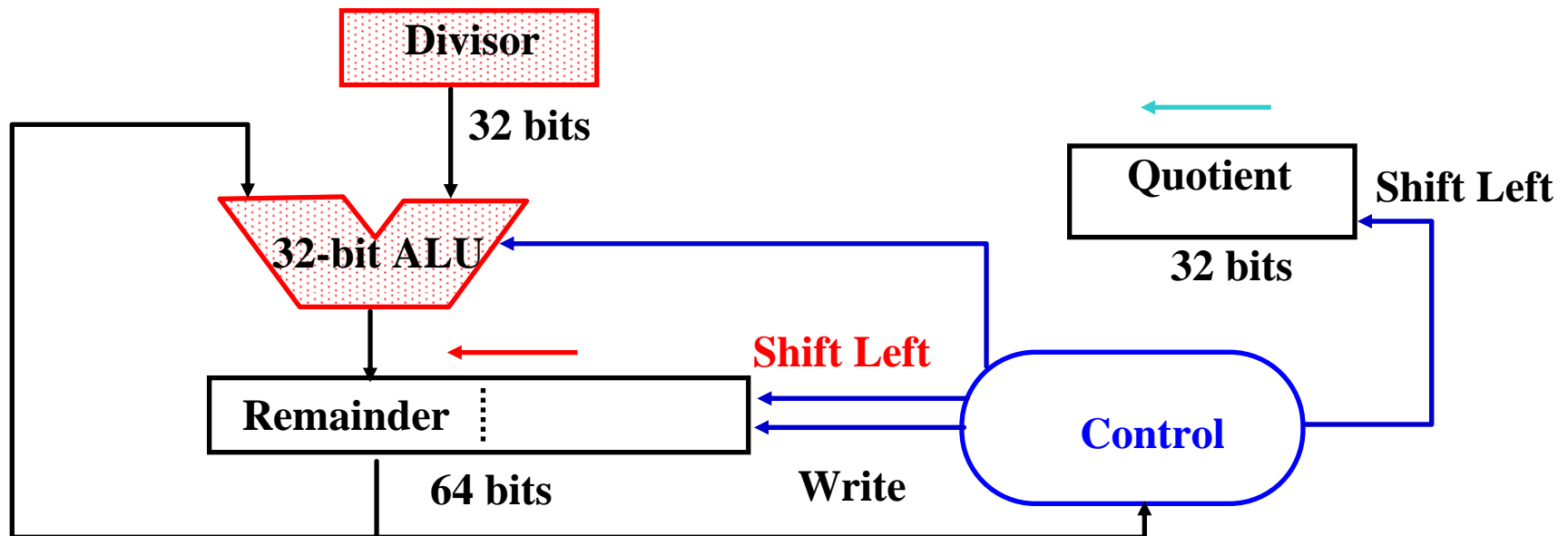
# DIVIDE HARDWARE Version 2

- ◆ 32-bit Divisor reg, 32-bit ALU, 64-bit Remainder reg, 32-bit Quotient reg



# Divide Algorithm Version 2

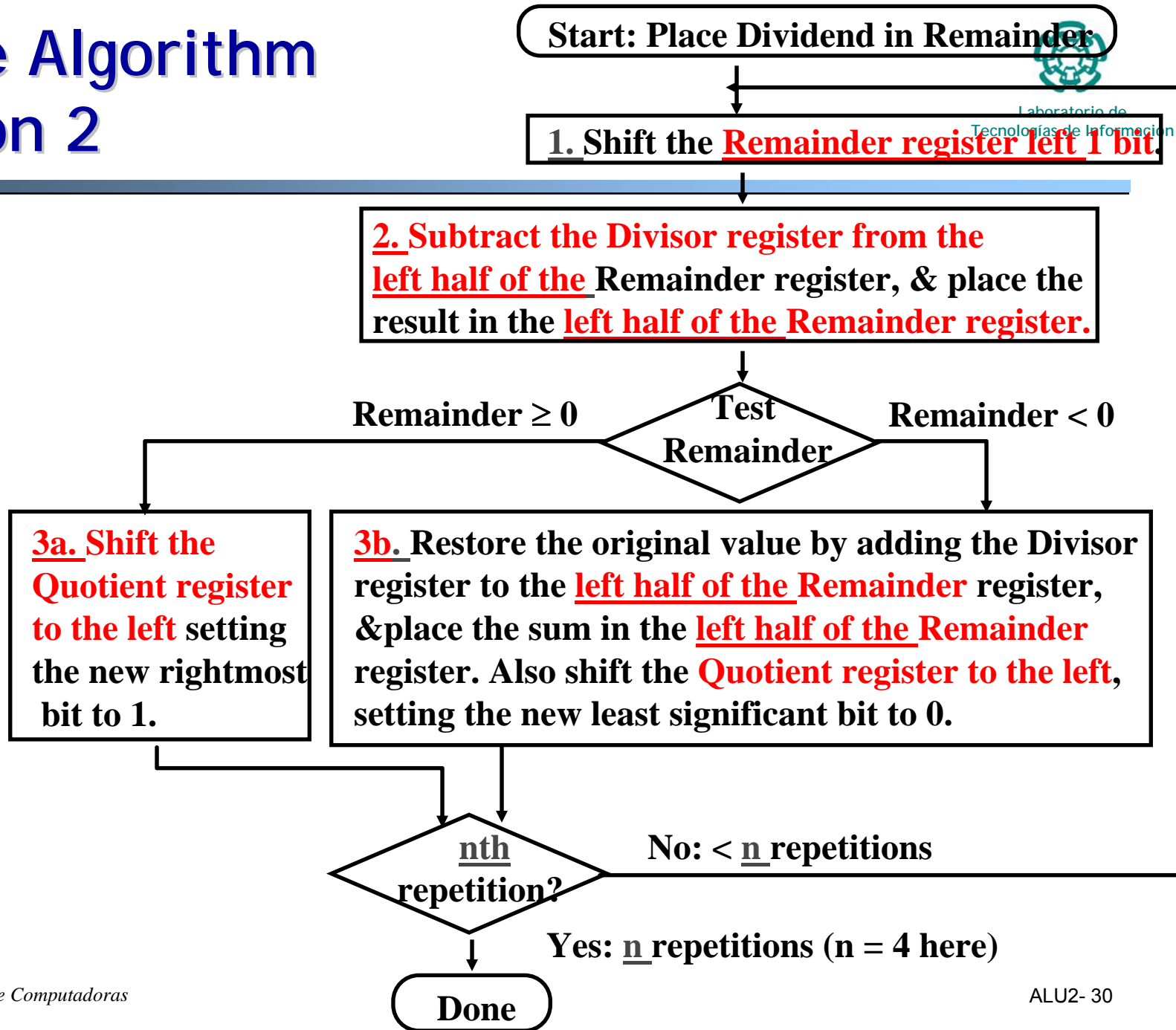

# Divide Algorithm

## Version 2



	Quotient	Divisor	Remainder	
0: Initial Values	0000	0010	0000	0111
1: sll Rem<-0	0000	0010	0000	1110
2: Rem = Rem-Div;	0000	0010	1110	1110
3b:Rem<0; Rem+=Div;sll Q<-0	0000	0010	0000	1110
1: sll Rem<-0	0000	0010	0001	1100
2: Rem = Rem-Div;	0000	0010	1111	1100
3b:Rem<0; Rem+=Div;sll Q<-0	0000	0010	0001	1100
1: sll Rem<-0	0000	0010	0011	1000
2: Rem = Rem-Div;	0000	0010	0001	1000
3a:Rem>0; sll Q<-1	0001	0010	0001	1000
1: sll Rem<-0	0001	0010	0011	0000
2: Rem = Rem-Div;	0001	0010	0001	0000
3a:Rem>0; sll Q<-1	0011	0010	0001	0000

# Observations on Divide Version 2



Laboratorio de  
Tecnologías de Información


- ◆ Eliminate Quotient register by combining with Remainder as shifted left
  - Start by shifting the Remainder left as before.
  - Thereafter loop contains only two steps because the shifting of the Remainder register shifts both the remainder in the left half and the quotient in the right half
  - The consequence of combining the two registers together and the new order of the operations in the loop is that the remainder will shifted left one time too many.
  - Thus the final correction step must shift back only the remainder in the left half of the register





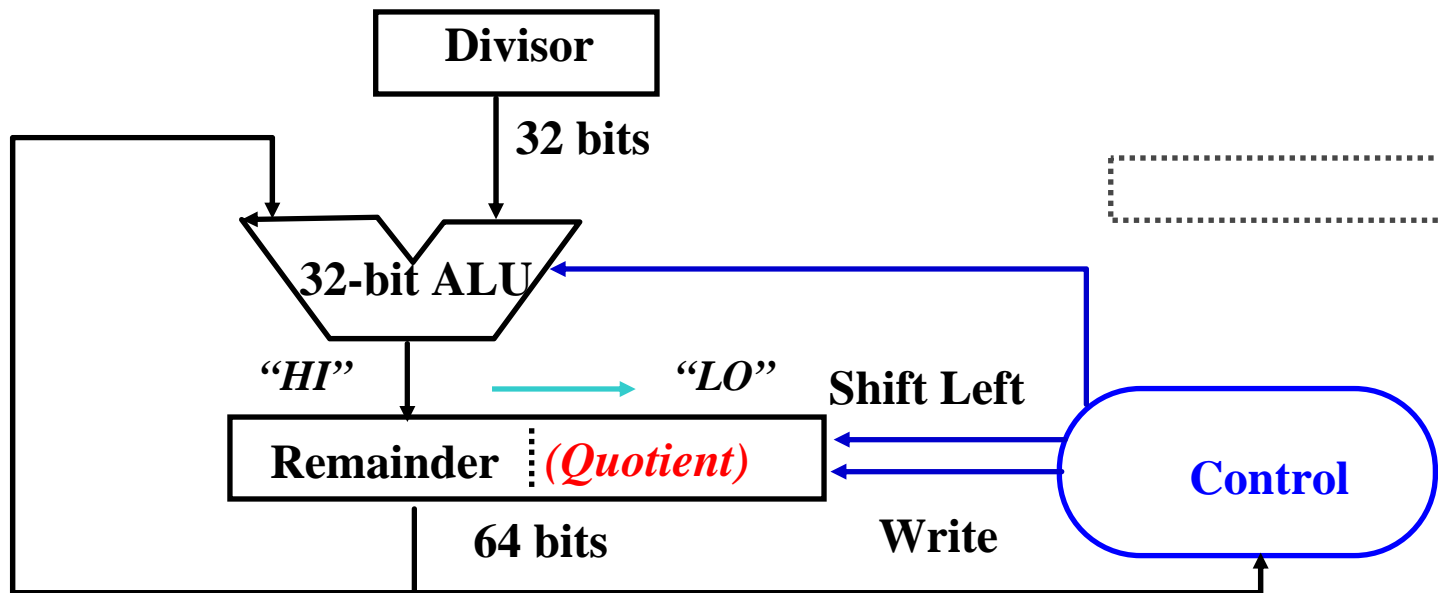
# DIVIDE HARDWARE Version 3

- ♦ 32-bit Divisor reg, 32-bit ALU, 64-bit Remainder reg, (0-bit Quotient reg)



# Divide Algorithm Version 3

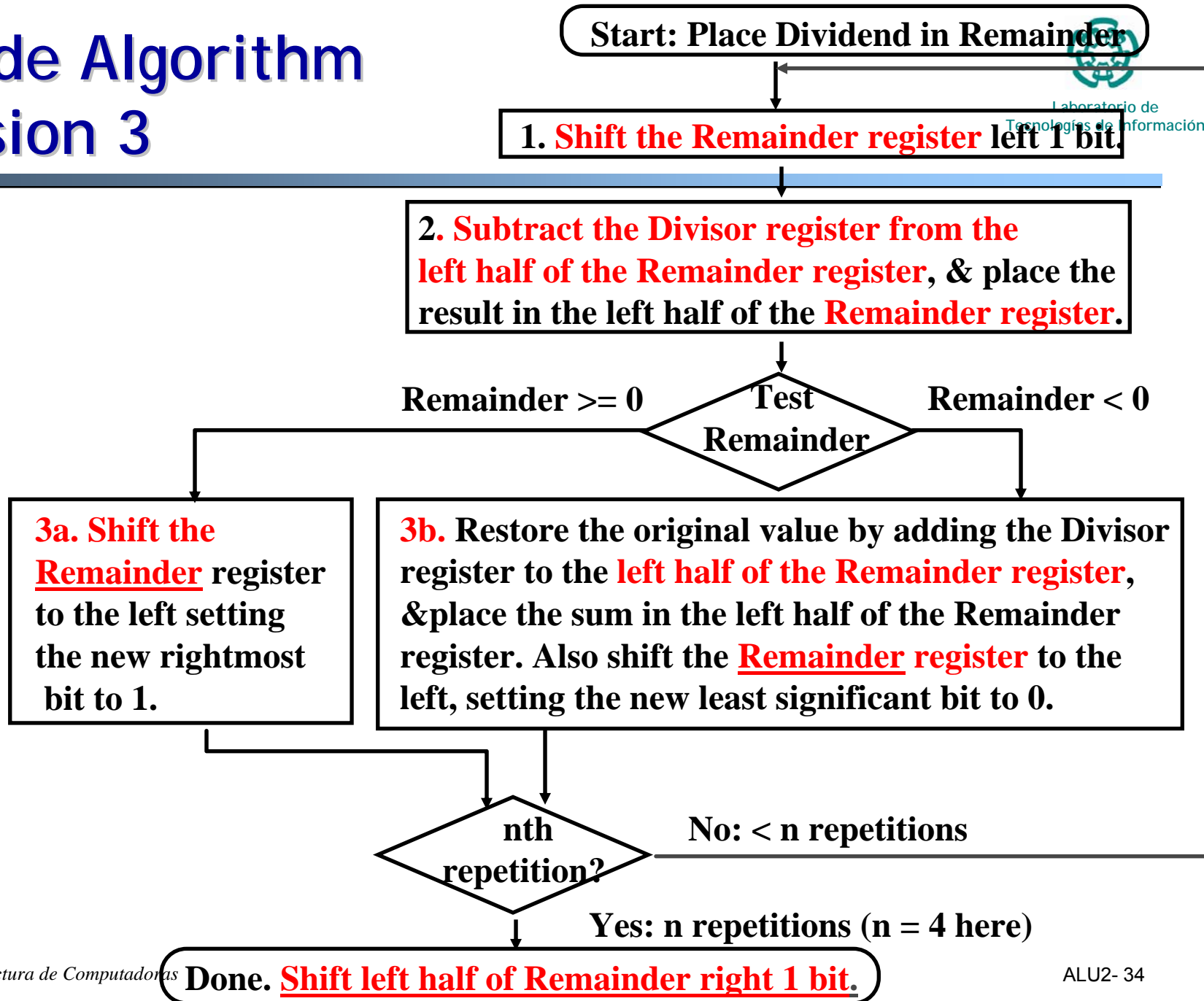

# Divide Algorithm Version 3



Laboratorio de  
Tecnologías de Información

```

0: Initial Values
1: sll Rem<-0
2: Rem = Rem-Div;
3b:Rem<0; Rem+=Div;sll Rem<-0
1: sll Rem<-0
2: Rem = Rem-Div;
3b:Rem<0; Rem+=Div;sll Rem<-0
1: sll Rem<-0
2: Rem = Rem-Div;
3a:Rem>0; sll Rem<-1
1: sll Rem<-0
2: Rem = Rem-Div;
3a:Rem>0; sll Rem<-1
    
```

Divisor	Remainder
0010	0000 0111
0010	0000 1110
0010	①110 1110
0010	0000 1110
0010	0001 1100
0010	①111 1100
0010	0001 1100
0010	0011 1000
0010	①001 1000
0010	0001 1001
0010	0011 0010
0010	①001 0010
0010	0001 0011

# Observations on Divide Version 3



Laboratorio de  
Tecnologías de Información

- ◆ Same Hardware as Multiply: just need ALU to add or subtract, and 63-bit register to shift left or shift right
- ◆ Hi and Lo registers in MIPS combine to act as 64-bit register for multiply and divide
- ◆ Signed Divides: Simplest is to remember signs, make positive, and complement quotient and remainder if necessary
  - Note: Dividend and Remainder must have same sign
  - Note: Quotient negated if Divisor sign & Dividend sign disagree  
e.g.,  $-7 \div 2 = -3$ , remainder =  $-1$
- ◆ Possible for quotient to be too large: if divide 64-bit integer by 1, quotient is 64 bits (“called saturation”)

- ◆ Multiply: successive refinement to see final design
  - 32-bit Adder, 64-bit shift register, 32-bit Multiplicand Register
- ◆ Division: successive refinement to see final design
  - 32-bit Adder, 64-bit shift register, 32-bit Divisor Register



# Hw5: Assignments

1	Claudia Méndez Garza	Design an 8-bit carry look ahead adder Develop equations Draw a schematic Indicate delays
2	José Ramírez Uresti	Design a <b>signed</b> 8x8 multiplier + times +, - times - + times -, - times +
3	Víctor Echeverría Ríos	Design a <b>signed</b> 8x8 divider + times +, - times - + times -, - times +

- ◆ Prepare a ppt presentation explaining the design and send it by e-mail
- ◆ **Due date: October 13th, 2007.**